

Mini-MIPS

From Weste/Harris
CMOS VLSI Design

1

Based on MIPS

- ◆ In fact, it's based on the multi-cycle MIPS from Patterson and Hennessy
 - Your CS/EE 3810 book...
- ◆ 8-bit version
 - 8-bit data and address
 - 32-bit instruction format
 - 8 registers numbered \$0-\$7
 - \$0 is hardwired to the value 0

CS/EE 3710

2

Instruction Set

Table 1.7 MIPS instruction set (subset supported)

Instruction	Function	Encoding	op	funct
add \$1, \$2, \$3	addition: $\$1 \leftarrow \$2 + \$3$	R	000000	100000
sub \$1, \$2, \$3	subtraction: $\$1 \leftarrow \$2 - \$3$	R	000000	100010
and \$1, \$2, \$3	bitwise and: $\$1 \leftarrow \$2 \text{ and } \$3$	R	000000	100100
or \$1, \$2, \$3	bitwise or: $\$1 \leftarrow \$2 \text{ or } \$3$	R	000000	100101
slt \$1, \$2, \$3	set less than: $\$1 \leftarrow 1 \text{ if } \$2 < \$3$ $\$1 \leftarrow 0 \text{ otherwise}$	R	000000	101010
addi \$1, \$2, imm	add immediate: $\$1 \leftarrow \$2 + \text{imm}$	I	001000	n/a
beq \$1, \$2, imm	branch if equal: $\text{PC} \leftarrow \text{PC} + \text{imm}^a$	I	000100	n/a
j destination	jump: $\text{PC} \leftarrow \text{destination}^a$	J	000010	n/a
lb \$1, imm(\$2)	load byte: $\$1 \leftarrow \text{mem}[\$2 + \text{imm}]$	I	100000	n/a
sb \$1, imm(\$2)	store byte: $\text{mem}[\$2 + \text{imm}] \leftarrow \1	I	101000	n/a

a. Technically, MIPS addresses specify bytes. Instructions require a four-byte word and must begin at addresses that are a multiple of four. To most effectively use instruction bits in the full 32-bit MIPS architecture, branch and jump constants are specified in words and must be multiplied by four (shifted left two bits) to be converted to byte addresses.

CS/EE 3710

3

Instruction Encoding

Format	Example	Encoding					
R	add \$rd, \$ra, \$rb	6	5	5	5	5	6
		0	ra	rb	rd	0	funct
I	beq \$ra, \$rb, imm	6	5	5	16		
		op	ra	rb	imm		
J	j dest	6	26				
		op	dest				

FIG 1.49 Instruction encoding formats

CS/EE 3710

4

Fibonacci C-Code

```
int fib(void)
{
    int n = 8;           /* compute nth Fibonacci number */
    int f1 = 1, f2 = -1; /* last two Fibonacci numbers */

    while (n != 0) {      /* count down to n = 0 */
        f1 = f1 + f2;
        f2 = f1 - f2;
        n = n - 1;
    }
    return f1;
}
```

FIG 1.50 C code for Fibonacci program

CS/EE 3710

5

Fibonacci C-Code

```
int fib(void)
{
    int n = 8;           /* compute nth Fibonacci number */
    int f1 = 1, f2 = -1; /* last two Fibonacci numbers */

    while (n != 0) {      /* count down to n = 0 */
        f1 = f1 + f2;
        f2 = f1 - f2;
        n = n - 1;
    }
    return f1;
}
```

FIG 1.50 C code for Fibonacci program

Cycle 1: $f1 = 1 + (-1) = 0$, $f2 = 0 - (-1) = 1$
Cycle 2: $f1 = 0 + 1 = 1$, $f2 = 1 - 1 = 0$
Cycle 3: $f1 = 1 + 0 = 1$, $f2 = 1 - 0 = 1$
Cycle 4: $f1 = 1 + 1 = 2$, $f2 = 2 - 1 = 1$
Cycle 5: $f1 = 2 + 1 = 3$, $f2 = 3 - 1 = 2$
Cycle 6: $f1 = 3 + 2 = 5$, $f2 = 5 - 2 = 3$

6

Fibonacci Assembly Code

```
# fib.asm
# Register usage: $3: n $4: f1 $5: f2
# return value written to address 255
fib:  addi $3, $0, 8      # initialize n=8
      addi $4, $0, 1      # initialize f1 = 1
      addi $5, $0, -1     # initialize f2 = -1
loop: beq $3, $0, end     # Done with loop if n = 0
      add $4, $4, $5      # f1 = f1 + f2
      sub $5, $4, $5      # f2 = f1 - f2
      addi $3, $3, -1     # n = n - 1
      j loop              # repeat until done
end:  sb $4, 255($0)      # store result in address 255
```

FIG 1.51 Assembly language code for Fibonacci program

Compute 8th Fibonacci number (8'd13 or 8'h0D)
Store that number in memory location 255

CS/EE 3710

7

Fibonacci Machine Code

Instruction	Binary Encoding	Hexadecimal Encoding
addi \$3, \$0, 8	001000 00000 00011 00000000000001000	20030008
addi \$4, \$0, 1	001000 00000 00100 00000000000000001	20040001
addi \$5, \$0, -1	001000 00000 00101 11111111111111111	2005ffff
beq \$3, \$0, end	000100 00011 00000 00000000000000101	10600004
add \$4, \$4, \$5	000000 00100 00101 00100 00000 100000	00852020
sub \$5, \$4, \$5	000000 00100 00101 00101 00000 100010	00852822
addi \$3, \$3, -1	001000 00011 00011 11111111111111111	2063ffff
j loop	000010 00000000000000000000000000011	08000003
sb \$4, 255(\$0)	101000 00000 00100 00000000111111111	a00400ff

FIG 1.52 Machine language code for Fibonacci program

Assembly Code

Machine Code

CS/EE 3710

8

Architecture

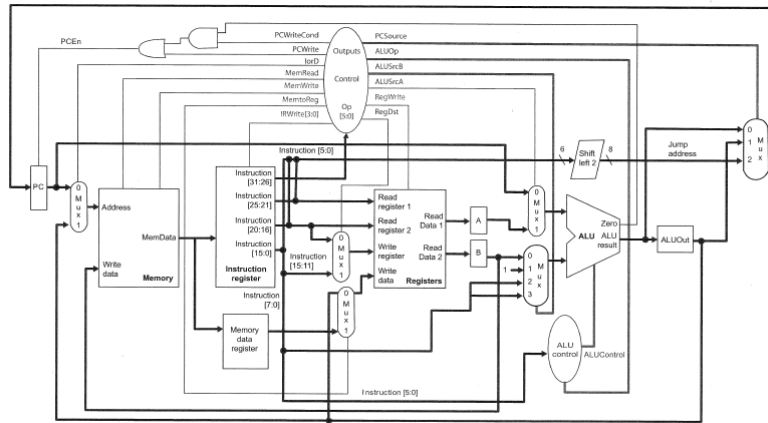


FIG 1.53 Multicycle MIPS microarchitecture. Reprinted from [Patterson04] with permission from Elsevier.

CS/EE 3710

9

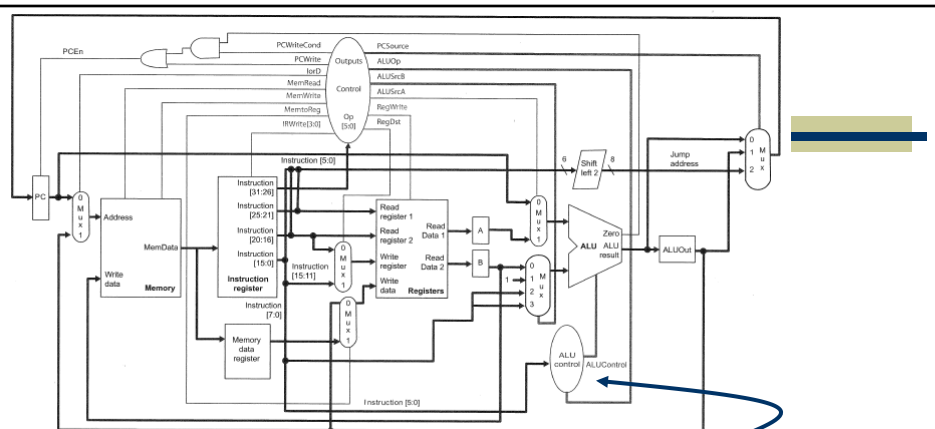


FIG 1.53 Multicycle MIPS microarchitecture. Reprinted from [Patterson04]

address
beq
R-type

Won't happen...

CS/EE 3710

Table 1.8 ALUControl determination

aluop	funct	alucontrol	Meaning
00	x	010	ADD
01	x	110	SUB
10	100000	010	ADD
10	100010	110	SUB
10	100100	000	AND
10	100101	001	OR
10	101010	111	SLT
11	x	x	undefined

10

Another View


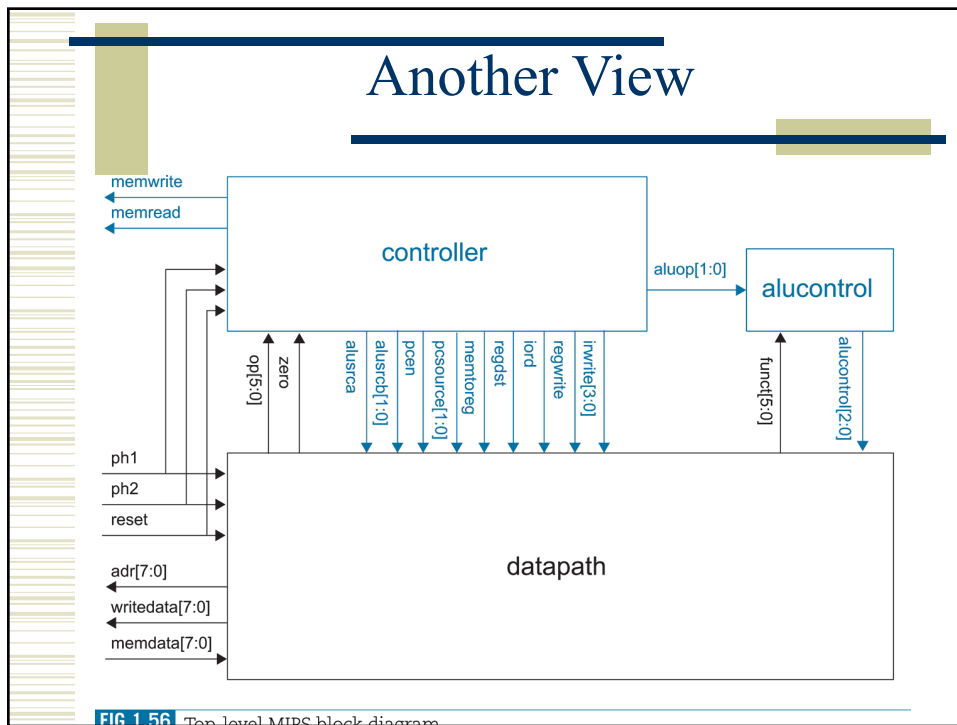


FIG 1.56 Top-level MIPS block diagram

11

Control FSM

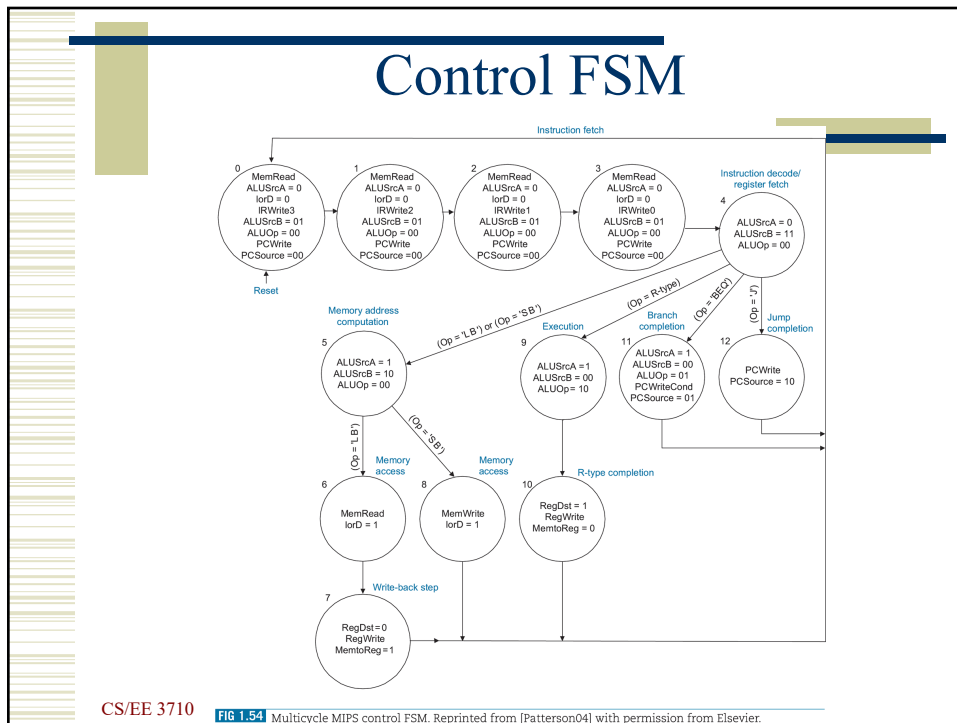

CS/EE 3710

FIG 1.54 Multicycle MIPS control FSM. Reprinted from [Patterson04] with permission from Elsevier

12

Connection to External Memory

Table 1.9 Top-level inputs and outputs

Inputs	Outputs
ph1	adr[7:0]
ph2	writedata[7:0]
reset	memread
memdata[7:0]	memwrite

 


FIG 1.55 MIPS computer system

13

External Memory from Book

```
// external memory accessed by MIPS
module exmemory #(parameter WIDTH = 8)
  (input      clk,
   input      memwrite,
   input  [WIDTH-1:0] adr, writedata,
   output reg [WIDTH-1:0] memdata);

  reg [31:0] RAM [(1<<WIDTH-2)-1:0];
  wire [31:0] word;

  // Initialize memory with program
  initial $readmemh("memfile.dat",RAM);

  // read and write bytes from 32-bit word
  always @(posedge clk)
    if(memwrite)
      case (adr[1:0])
        2'b00: RAM[adr>>2][7:0] <= writedata;
        2'b01: RAM[adr>>2][15:8] <= writedata;
        2'b10: RAM[adr>>2][23:16] <= writedata;
        2'b11: RAM[adr>>2][31:24] <= writedata;
      endcase
endmodule
```

```
assign word = RAM[adr>>2];
always @(*)
  case (adr[1:0])
    2'b00: memdata <= word[7:0];
    2'b01: memdata <= word[15:8];
    2'b10: memdata <= word[23:16];
    2'b11: memdata <= word[31:24];
  endcase
endmodule
```

Notes:

- Endianness is fixed here
- Writes are on posedge clk
- Reads are asynchronous
- This is a 32-bit wide RAM
- With 64 locations
- But with an 8-bit interface...

14

External memory on FPGA

```
module exmem #(parameter DATA_WIDTH=8, parameter ADDR_WIDTH=8)
  ( input [(DATA_WIDTH-1):0] data,
    input [(ADDR_WIDTH-1):0] addr,
    input we, clk,
    output [(DATA_WIDTH-1):0] q );
  // Declare the RAM variable
  reg [DATA_WIDTH-1:0] ram[2**ADDR_WIDTH-1:0];
  // Variable to hold the read address
  reg [ADDR_WIDTH-1:0] addr_reg;
  always @ (posedge clk)
  begin
    // Write
    if (we) ram[addr] <= data;
    // register to hold the read address
    addr_reg <= addr;
  end
  assign q = ram[addr_reg];
endmodule // exmem
```

CS/EE 3710

- This is synthesized to a Block RAM on the FPGA
- It's 8-bits wide
- With 256 locations
- Both writes and reads are clocked

15

exmem.v

```
module exmem #(parameter DATA_WIDTH=8, parameter ADDR_WIDTH=8)
  ( input [(DATA_WIDTH-1):0] data,
    input [(ADDR_WIDTH-1):0] addr,
    input we, clk,
    output [(DATA_WIDTH-1):0] q );
  // Declare the RAM variable
  reg [DATA_WIDTH-1:0] ram[2**ADDR_WIDTH-1:0];
  // Variable to hold the read address
  reg [ADDR_WIDTH-1:0] addr_reg;
  always @ (posedge clk)
  begin
    // Write
    if (we) ram[addr] <= data;
    // register to hold the read address
    addr_reg <= addr;
  end
  assign q = ram[addr_reg];
endmodule // exmem
```

CS/EE 3710

This is synthesized to a Block RAM on the FPGA

Note clock!

16


Memory Types on the FPGA

- ◆ DFFs available in Logic Array Blocks
 - Used mostly for local, unstructured memories
 - Used as DFFs in FSMs, local registers (regfile, flags, FSM control state variables, etc.)
- ◆ For more structured Memories, we use BLOCK RAMs (M10K)
 - Configurable w.r.t. operand word-lengths, and memory words
 - Use as RAMs, as well as ROMs

CS/EE 3710

17


FPGA Overview

 

CS/EE 3710

18

Adaptive Logic Modules (ALMs)

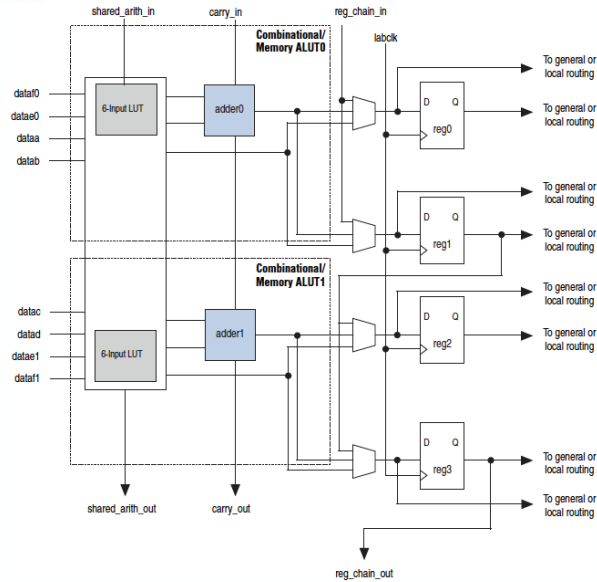

CS/EE 3710

19

Cyclone V SE 5CSEMA5F31C6

Table 4. Maximum Resource Counts for Cyclone V E Devices

Resource				Member Code				
		A2	A4		A5		A7	A9
Logic Elements (LE) (K)		25	4		77		150	301
ALM		9,430	18,860	30	29,080		56,480	113,560
Register		37,736	73,472	30	116,320		25,920	454,240
Memory (Kb)	M10K	1,760	3,520	0	4,460		6,860	12,200
	MLAB	196	392		424		836	1,717
Variable-precision DSP Block		25	6		150		156	342
18 x 18 Multiplier		50	12		300		312	684
PLL		4	1		6		7	8
GPIO		224	22		240		480	480
LVDS	Transmitter	56	5		60		120	120
	Receiver	56	5		60		120	120
Hard Memory Controller		1	1		2		2	2

20

M10K RAM Blocks

- ♦ M10K = 10K bits = $10 \times 1024 = 10,240$ bits
 - 397 blocks = $397 \times 10\text{K}$ bits total

Table 19. Supported Embedded Memory Block Configurations for Cyclone V Devices

This table lists the maximum configurations supported for the embedded memory blocks. The information is applicable only to the single-port RAM and ROM modes.

Memory Block	Depth (bits)	Programmable Width
MLAB	32	x16, x18, or x20
M10K	256	x40 or x32
	512	x20 or x16
	1K	x10 or x8
	2K	x5 or x4
	4K	x2
	8K	x1

CS/EE 3710

21

Looking Ahead

- ♦ Project has 16bit words
 - 512x16 is one M10K configuration
 - 397 blocks = 203,264 words
 - $2^{16} = 65,535$ words
 - $2^{18} = 262,144$
- ♦ So, maybe you could use an 18-bit address with the 16-bit data word?
 - That's what the CR-16 does...

CS/EE 3710

22

Synchronous RAM

Table 5. Write and Read Operations Triggering for Embedded Memory Blocks

This table lists the write and read operations triggering for various embedded memory blocks.

Embedded Memory Blocks	Write Operation	Read Operation
M10K	Rising clock edges	Rising clock edges

- ♦ Single Port: one read or one write per cycle
 - Synchronous with rising clock edge
- ♦ Dual Port
 - Two reads or two writes per cycle
 - Can even support different clocks on each port

CS/EE 3710

23

exmem.v

```

module exmem #(parameter DATA_WIDTH=8, parameter ADDR_WIDTH=8)
( input [(DATA_WIDTH-1):0] data,
  input [(ADDR_WIDTH-1):0] addr,
  input we, clk,
  output [(DATA_WIDTH-1):0] q );
// Declare the RAM variable
reg [DATA_WIDTH-1:0] ram[2**ADDR_WIDTH-1:0];
// Variable to hold the read address
reg [ADDR_WIDTH-1:0] addr_reg;
always @ (posedge clk)
begin
    // Write
    if (we) ram[addr] <= data;
    // register to hold the read address
    addr_reg <= addr;
end
assign q = ram[addr_reg];
endmodule // exmem
    
```

Addr_reg is stored
on rising edge

So, Read happens
using stored address

CS/EE 3710

24

Recall – Overall System

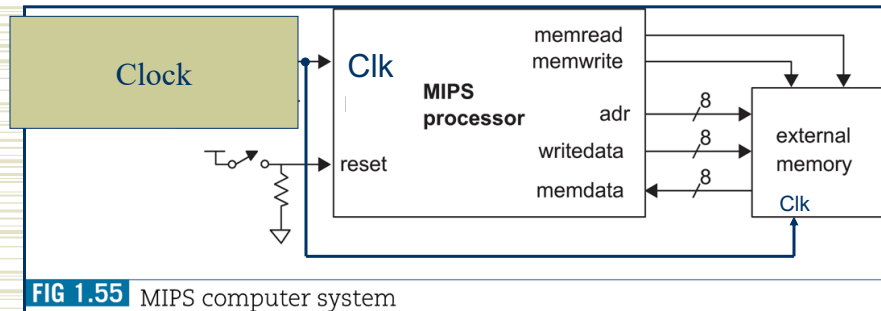


FIG 1.55 MIPS computer system

CS/EE 3710

25

Recall – Overall System

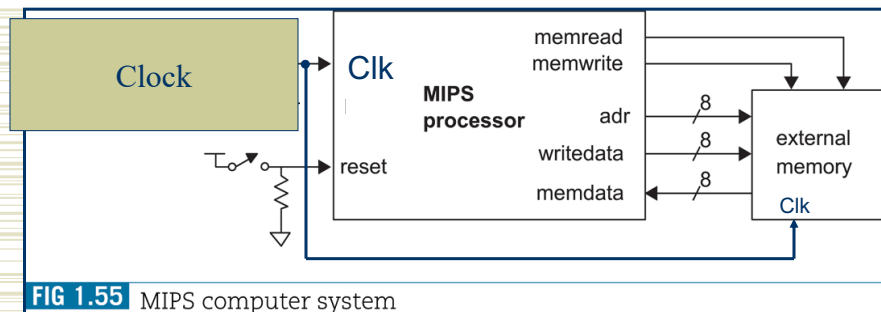


FIG 1.55 MIPS computer system

So, what are the implications of using a RAM that has both clocked reads and writes instead of clocked writes and async reads? (we'll come back to this question...)

CS/EE 3710

26

mips Block Diagram

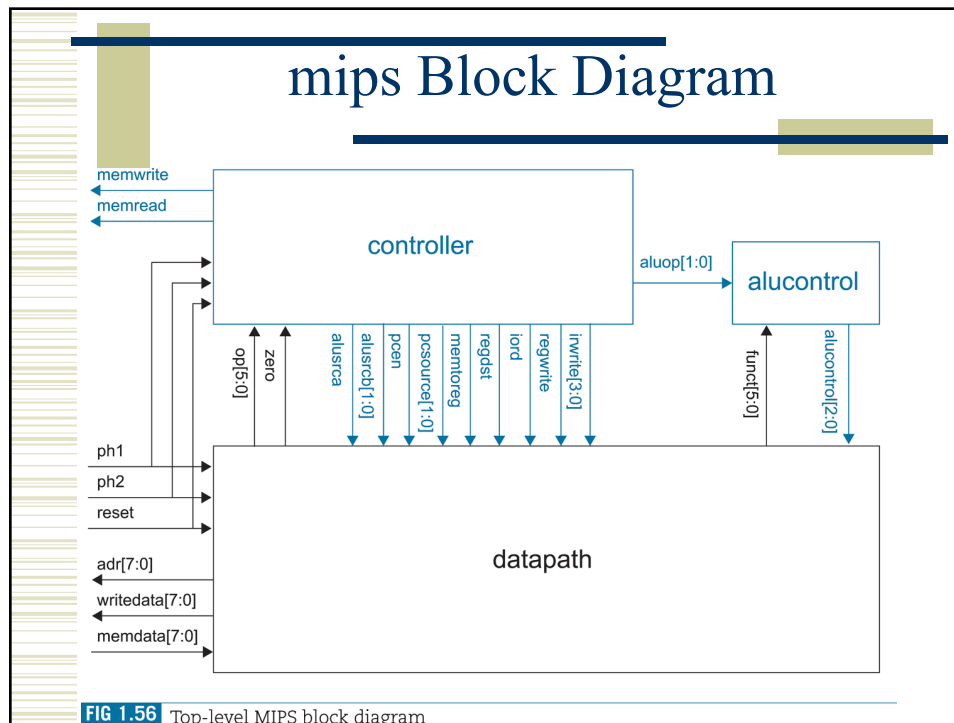


FIG 1.56 Top-level MIPS block diagram

27

mips.v

```
// simplified MIPS processor
module mips #(parameter WIDTH = 8, REGBITS = 3)
    (input      clk, reset,
     input [WIDTH-1:0] memdata,
     output     memread, memwrite,
     output [WIDTH-1:0] adr, writedata);

    wire [31:0] instr;
    wire      zero, alusca, memtoereg, iord, pcen, regwrite, regdst;
    wire [1:0] aluop, pcsource, alusrcb;
    wire [3:0] irwrite;
    wire [2:0] alucont;

    controller cont(clk, reset, instr[31:26], zero, memread, memwrite,
                   alusca, memtoereg, iord, pcen, regwrite, regdst,
                   pcsource, alusrcb, aluop, irwrite);
    alucontrol ac(aluop, instr[5:0], alucont);
    datapath dp(WIDTH, REGBITS)
        dp(clk, reset, memdata, alusca, memtoereg, iord, pcen,
           regwrite, regdst, pcsource, alusrcb, irwrite, alucont,
           zero, instr, adr, writedata);
endmodule
```

28

Controller

```

module controller(input clk, reset,
                 input [5:0] op,
                 input zero,
                 output reg memread, memwrite, alusrcA, memtoReg, iord,
                 output pcen,
                 output reg regwrite, regdst,
                 output reg [1:0] pcsource, alusrcB, aluop,
                 output reg [3:0] inwrite);

```

```

parameter FETCH1 = 4'b0001;
parameter FETCH2 = 4'b0010;
parameter FETCH3 = 4'b0011;
parameter FETCH4 = 4'b0100;
parameter DECODE = 4'b0101;
parameter MEMADR = 4'b0110;
parameter LBRD = 4'b0111;
parameter LBRW = 4'b1000;
parameter SBWR = 4'b1001;
parameter RTYPEEX = 4'b1010;
parameter RTYPEENR = 4'b1011;
parameter BEQEX = 4'b1100;
parameter JEX = 4'b1101;

```

State Codes

```

parameter LB = 6'b100000;
parameter SB = 6'b101000;
parameter RTYPE = 6'b0;
parameter BEQ = 6'b000100;
parameter J = 6'b000010;

```

Useful constants to compare against

```

reg [3:0] state, nextstate;
reg pcwrite, pcwritecond;


// state register
always @(posedge clk)
if(reset) state <= FETCH1;
else state <= nextstate;

```

State Register

29

Control FSM

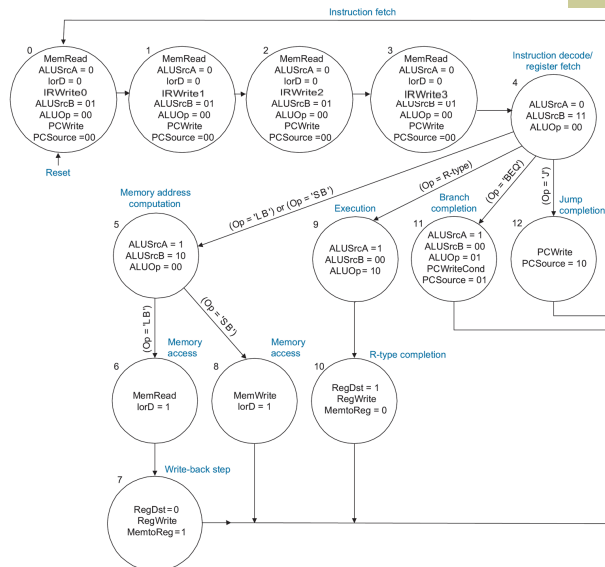

CS/EE 3710

FIG 1.54 Multicycle MIPS control FSM. Reprinted from [Patterson04] with permission from Elsevier.

30

Next State Logic

```
// next state logic
always @(*)
begin
    case(state)
        FETCH1: nextstate <= FETCH2;
        FETCH2: nextstate <= FETCH3;
        FETCH3: nextstate <= FETCH4;
        FETCH4: nextstate <= DECODE;
        DECODE: case(op)
            LB: nextstate <= MEMADR;
            SB: nextstate <= MEMADR;
            RTYPE: nextstate <= RTYPEEX;
            BEQ: nextstate <= BEQEX;
            J: nextstate <= JEX;
            default: nextstate <= FETCH1; // should never happen
        endcase
        MEMADR: case(op)
            LB: nextstate <= LBRD;
            SB: nextstate <= SBWR;
            default: nextstate <= FETCH1; // should never happen
        endcase
        LBRD: nextstate <= LBWR;
        LBWR: nextstate <= FETCH1;
        SBWR: nextstate <= FETCH1;
        RTYPEEX: nextstate <= RTYPEWR;
        RTYPEWR: nextstate <= FETCH1;
        BEQEX: nextstate <= FETCH1;
        JEX: nextstate <= FETCH1;
        default: nextstate <= FETCH1; // should never happen
    endcase
end
```

CS/EE 3710

31

Output Logic

```
always @(*)
begin
    // set all outputs to zero, then conditionally assert
    // just the appropriate ones
    irwrite <= 4'b0000;
    pcwrite <= 0; pcwritecond <= 0;
    regwrite <= 0; regdst <= 0;
    memread <= 0; memwrite <= 0;
    alusrcA <= 0; alusrcB <= 2'b00; aluop <= 2'b00;
    pcsource <= 2'b00;
    iord <= 0; memtoereg <= 0;
    case(state)
        FETCH1:
            begin
                memread <= 1;
                irwrite <= 4'b0001; // changed to reflect new memory and
                alusrcB <= 2'b01; // get the IR bits in the right spots
                pcwrite <= 1; // FETCH 2,3,4 also changed...
            end
        FETCH2:
            begin
                memread <= 1;
                irwrite <= 4'b0010;
                alusrcB <= 2'b01;
                pcwrite <= 1;
            end
        FETCH3:
            begin
                memread <= 1;
                irwrite <= 4'b0100;
                alusrcB <= 2'b01;
                pcwrite <= 1;
            end
    end
```

Very common way
to deal with default
values in combinational
Always blocks

Continued for the other states...

32

Output Logic

```

    SBWR:
    begin
        memwrite <= 1;
        iord <= 1;
    end
    RTYPEEX:
    begin
        alusrca <= 1;
        aluop <= 2'b10;
    end
    RTYPEWR:
    begin
        regdst <= 1;
        regwrite <= 1;
    end
    BEQEX:
    begin
        alusrca <= 1;
        aluop <= 2'b01;
        pcwritecond <= 1;
        pcsource <= 2'b01;
    end
    JEX:
    begin
        pcwrite <= 1;
        pcsource <= 2'b10;
    end
endcase
end
assign pcen = pcwrite | (pcwritecond & zero); // program counter enable
endmodule

```

Two places to update the PC
pcwrite on jump
pcwritecond on BEQ

Why AND these two?

33

ALU Control

```

module alucontrol(input [1:0] aluop,
                  input [5:0] funct,
                  output reg [2:0] alucont);

    always @(*)
    case(aluop)
        2'b00: alucont <= 3'b010; // add for lb/sb/addi
        2'b01: alucont <= 3'b110; // sub (for beq)
        default: case(funct) // R-Type instructions
            6'b100000: alucont <= 3'b010; // add (for add)
            6'b100010: alucont <= 3'b110; // subtract (for sub)
            6'b100100: alucont <= 3'b000; // logical and (for and)
            6'b100101: alucont <= 3'b001; // logical or (for or)
            6'b101010: alucont <= 3'b111; // set on less (for slt)
            default: alucont <= 3'b101; // should never happen
        endcase
    endcase
endmodule

```

Table 1.8 ALUControl determination

	aluop	funct	alucontrol	Meaning
address	00	x	010	ADD
beq	01	x	110	SUB
R-type	10	100000	010	ADD
	10	100010	110	SUB
	10	100100	000	AND
	10	100101	001	OR
	10	101010	111	SLT
	11	x	x	undefined

CS/EE 3710

Won't happen...

34

ALU

```
module alu #(parameter WIDTH = 8)
  (input  [WIDTH-1:0] a, b,
   input  [2:0]      alucont,
   output reg [WIDTH-1:0] result);

  wire [WIDTH-1:0] b2, sum, slt;

  assign b2 = alucont[2] ? ~b:b;
  assign sum = a + b2 + alucont[2];
  // slt should be 1 if most significant bit of sum is 1
  assign slt = sum[WIDTH-1];

  always@(*)
    case(alucont[1:0])
      2'b00: result <= a & b;
      2'b01: result <= a | b;
      2'b10: result <= sum;
      2'b11: result <= slt;
    endcase
endmodule
```

Invert b if subtract...

add is $a + b$
sub is $a + \sim b + 1$

subtract on slt
then check if answer is negative

CS/EE 3710

35

zerodetect

```
module zerodetect #(parameter WIDTH = 8)
  (input [WIDTH-1:0] a,
   output y);

  assign y = (a==0);
endmodule
```

CS/EE 3710

36

Register File

```
module regfile #(parameter WIDTH = 8, REGBITS = 3)
    (input          clk,
     input          regwrite,
     input  [REGBITS-1:0] ra1, ra2, wa,
     input  [WIDTH-1:0]   wd,
     output [WIDTH-1:0]   rd1, rd2);

    reg  [WIDTH-1:0] RAM [(1<<REGBITS)-1:0];

    // three ported register file
    // read two ports combinational
    // write third port on rising edge of clock
    // register 0 hardwired to 0
    always @(posedge clk)
        if (regwrite) RAM[wa] <= wd;

    assign rd1 = ra1 ? RAM[ra1] : 0;
    assign rd2 = ra2 ? RAM[ra2] : 0;
endmodule
```

What is this synthesized into?

CS/EE 3710

37

Datapath

```
module datapath #(parameter WIDTH = 8, REGBITS = 3)
    (input          clk, reset,
     input  [WIDTH-1:0] memdata,
     input          alusrc, memtoreg, iord,
     input          pcen, regwrite, regdst,
     input  [1:0]    pcsource, alusrcb,
     input  [3:0]    irwrite,
     input  [2:0]    alucont,
     output         zero,
     output [31:0]   instr,
     output [WIDTH-1:0] adr, writedata);

    // the size of the parameters must be changed to match the WIDTH parameter
    localparam CONST_ZERO = 8'b0;
    localparam CONST_ONE  = 8'b1;

    wire [REGBITS-1:0] ra1, ra2, wa;
    wire [WIDTH-1:0]   pc, nextpc, md, rd1, rd2, wd, a, src1, src2, alurest,
                    aluout, constx4;

    // shift left constant field by 2
    assign constx4 = {instr[WIDTH-3:0], 2'b00};

    // register file address fields
    assign ra1 = instr[REGBITS+20:21];
    assign ra2 = instr[REGBITS+15:16];
    mux2      #(REGBITS) regmux(instr[REGBITS+15:16], instr[REGBITS+10:11], regdst, wa);

    // independent of bit width, load instruction into four
    // 8-bit registers over four cycles
    flopen  #(8)  ir0(clk, irwrite[0], memdata[7:0], instr[7:0]);
    flopen  #(8)  ir1(clk, irwrite[1], memdata[7:0], instr[15:8]);
    flopen  #(8)  ir2(clk, irwrite[2], memdata[7:0], instr[23:16]);
    flopen  #(8)  ir3(clk, irwrite[3], memdata[7:0], instr[31:24]);
```

Fairly complex...

Not really, but it does have lots of registers instantiated directly

It also instantiates muxes...


Instruction Register

38

Datapath continued

```
// datapath
flopennr #(WIDTH) pcreg(clk, reset, pcen, nextpc, pc);
flop #(WIDTH) mdr(clk, mdata, md);
flop #(WIDTH) areg(clk, rd1, a);
flop #(WIDTH) wrd(clk, rd2, wdata);
flop #(WIDTH) res(clk, aluresult, aluout);
mux2 #(WIDTH) admux(pc, aluout, iord, adr);
mux2 #(WIDTH) src1mux(pc, a, alusrc1, src1);
mux4 #(WIDTH) src2mux(wdata, CONST_ONE, instr[WIDTH-1:0],
    constx4, alusrcb, src2);
mux4 #(WIDTH) pcmux(aluresult, aluout, constx4, CONST_ZERO, pcsource, nextpc);
mux2 #(WIDTH) wdmux(aluout, md, memtoreg, wd);
regfile #(WIDTH, REGBITS) rf(clk, regwrite, ra1, ra2, wa, wd, rd1, rd2);
alu #(WIDTH) alunit(src1, src2, alucont, aluresult);
zerodetect #(WIDTH) zd(aluresult, zero);
endmodule
```

Flops and
muxes...

 

RF and
ALU

CS/EE 3710

FIGURE 3.10 Multicycle MIPS microarchitecture. Reprinted from [Patterson04] with permission from Elsevier.

39

Flops and MUXes

```
module flop #(parameter WIDTH = 8)
    (input clk,
     input [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);

    always @(posedge clk)
        q <= d;
endmodule

module flopenn #(parameter WIDTH = 8)
    (input clk, en,
     input [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);

    always @(posedge clk)
        if (en) q <= d;
endmodule

module flopennr #(parameter WIDTH = 8)
    (input clk, reset, en,
     input [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);

    always @(posedge clk)
        if (reset) q <= 0;
        else if (en) q <= d;
endmodule

module mux2 #(parameter WIDTH = 8)
    (input [WIDTH-1:0] d0, d1,
     input s,
     output [WIDTH-1:0] y);

    assign y = s ? d1 : d0;
endmodule

module mux4 #(parameter WIDTH = 8)
    (input [WIDTH-1:0] d0, d1, d2, d3,
     input [1:0] s,
     output reg [WIDTH-1:0] y);

    always @(*)
        case(s)
            2'b00: y <= d0;
            2'b01: y <= d1;
            2'b10: y <= d2;
            2'b11: y <= d3;
        endcase
endmodule
```

CS/EE 3710

40

Back to the Memory Question

- ♦ What are the implications of using RAM that is clocked on both write and read?
 - Book version was async read
 - So, let's look at the sequence of events that happen to read the instruction
 - Four steps – read four bytes and put them in four slots in the 32-bit instruction register (IR)

CS/EE 3710

41

Instruction Fetch


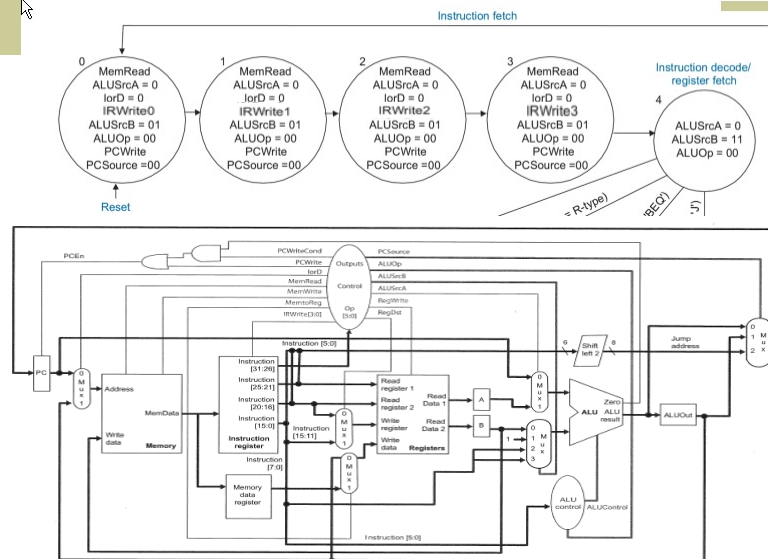


FIG 1.53 Multicycle MIPS microarchitecture. Reprinted from [Patterson04] with permission from Elsevier.

42

Instruction Fetch

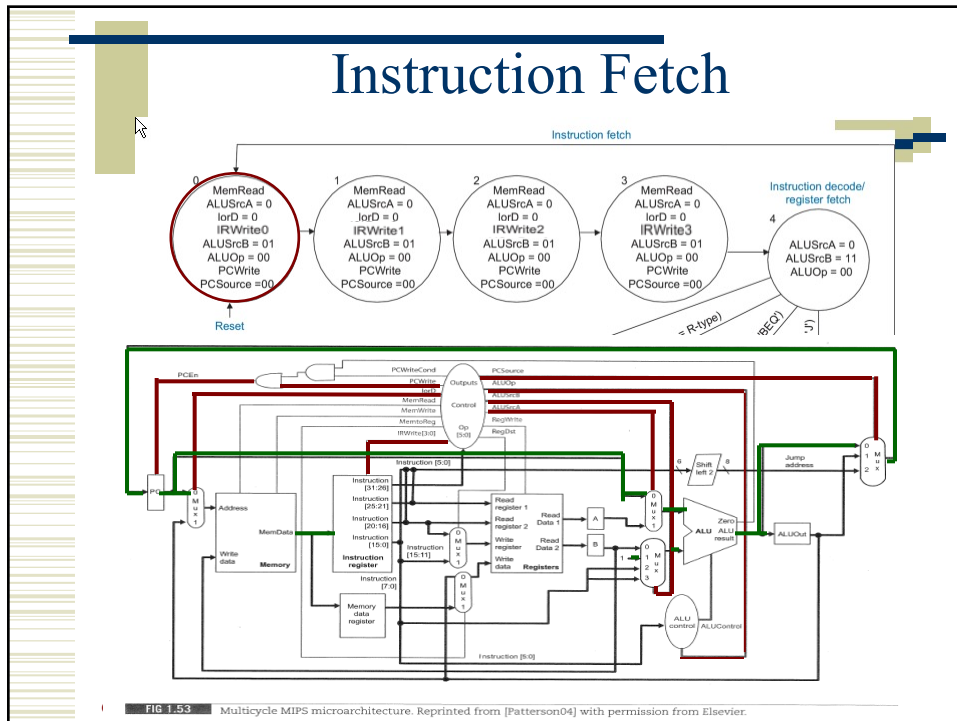

43

Instruction Fetch

```
// independent of bit width, load instruction into four
// 8-bit registers over four cycles
flopen  #(8)    ir0(clk, irwrite[0], memdata[7:0], instr[7:0]);
flopen  #(8)    ir1(clk, irwrite[1], memdata[7:0], instr[15:8]);
flopen  #(8)    ir2(clk, irwrite[2], memdata[7:0], instr[23:16]);
flopen  #(8)    ir3(clk, irwrite[3], memdata[7:0], instr[31:24]);
```

Instruction Register

```
module flopen #(parameter WIDTH = 8)
    (input          clk, en,
     input  [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);


    always @(posedge clk)
        if (en) q <= d;
endmodule
```

- Memread, irwrite, addr, etc are set up just after clk edge
- Data comes back sometime after that (async)
- Data is captured in ir0 – ir3 on the next rising clk edge
- **How does this change if reads are clocked?**

CS/EE 3710

44

mips + exmem

 

mips is expecting async reads

exmem has clocked reads

One of those rare cases where using both edges of the clock is useful!

Matches the behavior of the “two-phase clocks” described in the book...

CS/EE 3710

45


Memory Mapped I/O

- ◆ Break memory space into pieces (ranges)
 - For some of those pieces: regular memory
 - For some of those pieces: I/O
 - That is, reading from an address in that range results in getting data from an I/O device
 - Writing to an address in that range results in data going to an I/O device

CS/EE 3710

46

Mini-MIPS Memory Map

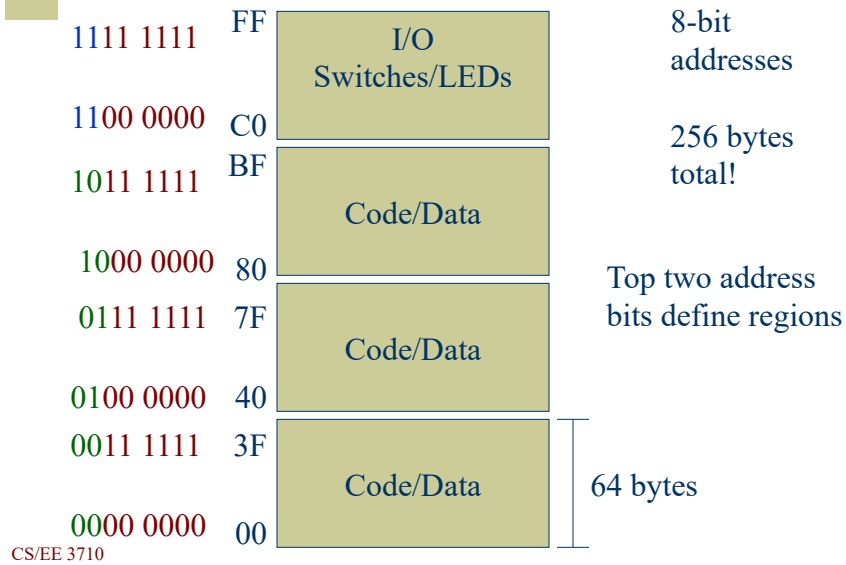

47

Enabled Devices

Only write to that device
(i.e. enable it) if you're
in the appropriate memory range.

Check top two address bits!

```
module flopen #(parameter WIDTH = 8)
  (input      clk, en,
   input  [WIDTH-1:0] d,
   output reg [WIDTH-1:0] q);

  always @(posedge clk)
    if (en) q <= d;
endmodule
```

CS/EE 3710

48

MUXes for Return Data

```
module mux2 #(parameter WIDTH = 8)
    (input [WIDTH-1:0] d0, d1,
     input s,
     output [WIDTH-1:0] y);

    assign y = s ? d1 : d0;
endmodule
```

Use MUX to decide if data is coming from memory or from I/O

Check address bits!

The diagram illustrates a processor core with the following components and connections:

- Instruction Register:** Receives instructions from the Instruction Memory (31:26, 25:21, 20:16, 15:0) and outputs them to the Instruction Memory (15:11, 7:0).
- Memory:** Receives data from the Memory data register and outputs it to the Memory data register.
- Memory data register:** Receives data from the Memory and outputs it to the Memory data register.
- Control Signals:** The Instruction Register outputs control signals (Op [5:0], IRWrite[3:0]) to the Memory and the Memory data register.
- MUX2 Module:** A custom module that selects between memory data and I/O data based on a control signal 's'. It is used to select between the Memory data register output and the I/O data (from the Instruction Register) to be sent to the Memory data register.

49

Mini-MIPS in a Nutshell

- ◆ Understand and simulate mips/exmem
 - Add **ADDI** instruction
 - Fibonacci program – correct if 8'0d is written to memory location 255
- ◆ Augment the system
 - Add memory mapped I/O to switches/LEDs
 - Or add simple mux switch for data return
 - Write new Fibonacci program
 - Simulate in ModelSim
 - Demonstrate on your board

CS/EE 3710

50

My Initial Testbench...

```


2
3 `timescale 1ns / 1ps
4
5 module mips_mem_mips_mem_sch_tb();
6
7 // Inputs
8 reg clk;
9 reg reset;
10
11 // Output
12 wire memread;
13
14 // Bidirs
15
16 // Instantiate the UUT
17 mips_mem UUT (
18     .clk(clk),
19     .memread(memread),
20     .reset(reset)
21 );
22 // Initialize Inputs
23 initial begin
24     reset <= 1;
25     #22 reset <= 0;
26     end
27
28 // Generate clock to sequence tests
29 always
30 begin
31     clk <= 1; # 5; clk <= 0; # 5;
32 end
33
34 // check the data on the memory interface between mips and exmem
35 // If you're writing, and the address is 255, then the data should
36 // be 8'h0d if you've computed the correct 8th Fibonacci number
37 always@ (negedge clk)
38 if (UUT.memwrite)
39 if (UUT.addr == 8'd255 & UUT.wdata == 8'h0d)
40     $display("Yay - Fibonacci completed successfully!");
41 else $display("Oops - wrong value written to addr 255: %h", UUT.wdata);
42

```

CS/EE 3710

51

My Initial Results

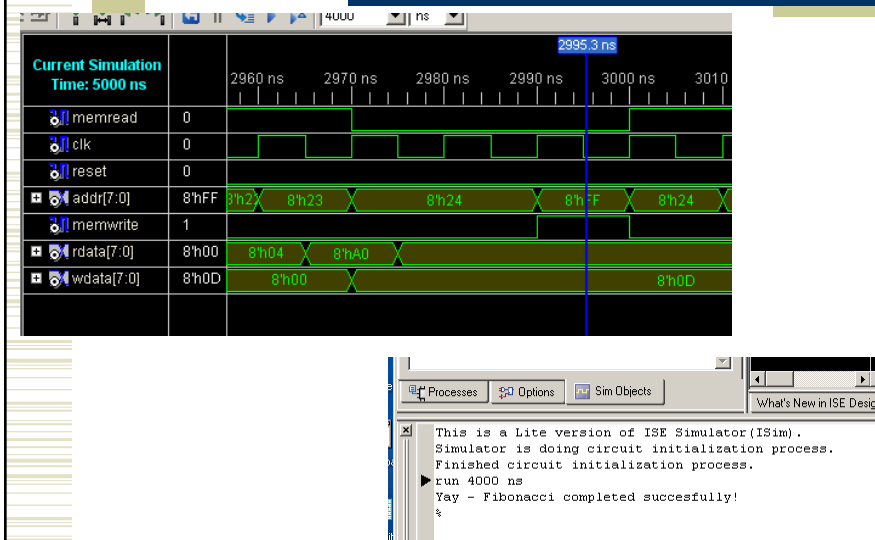

52